

Embedded Systems

Please indicate your **name**, **group number**, and **discussion slot tutor**. Only one submission per group is necessary.

Problem 1: VHDL 4-Bit Register

In hardware design, one usually uses a global clock signal to establish a discrete model of time. Figure 1 shows such a clock signal where each period between two rising edges represents a certain (discrete) moment of time. Using this abstraction, it is possible to describe the behaviour of circuits in terms of clock cycle indexes. Here, SIG^i denotes the stabilized value of signal SIG during the *first* half ($\text{clk} = 1$) of cycle i .

 


Figure 1: Timing diagram of a typical clock signal

An n -bit register is a standard circuit in hardware design that stores n -bit values. A register has an n -bit input IN , an 1-bit input EN , and an n -bit output OUT . It works as follows: whenever $EN = 1$ the register stores IN , OUT always gives the last value that has been stored in a previous cycle, even if $EN = 1$ in the current cycle. More formally, let IN^i , OUT^i , and EN^i be the input, output, and enabled signals of the i^{th} cycle, respectively, then the behaviour is defined as follows:

$$OUT^{i+1} = \begin{cases} IN^i, & \text{if } EN^i = 1 \\ OUT^i, & \text{otherwise} \end{cases}$$

The input and output interface of a 4-bit register is described by the following VHDL declaration:

```
entity register is
port(
```

```
    in3, in2, in1, in0, en, clk: in bit;
    out3, out2, out1, out0: out bit);
end register;
```

Note that `in0...in3` describe the individual input bits in this interface, and `out0...out3` describe the output bits. Start with this declaration to develop a 4-bit register in VHDL.

¹ When writing the structural architectures, you can use flip-flops and basic gates (NOT, AND, OR, NAND, XOR, NOR) as your starting subentities.

1. Write a VHDL *behavioral* architecture implementing a 4-bit register.
2. Write a VHDL *structural* architecture implementing a 4-bit register.

¹Note that `clk` is the clock signal whose rising edges define the cycles.